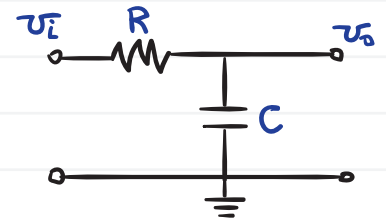


## First-order filter response

A passive first-order filter is an example of a measurement system (a signal conditioner) that is first-order with a (typically) sinusoidal forcing function.

## Low-pass filter response

The RC-circuit in the figure is often used as a low-pass filter.



## Circuit analysis

## Response analysis

This is a first-order ODE. If the circuit is being used as a filter, we usually characterize it in terms of its magnitude ratio  $M(\omega)$  and phase  $\phi$ , which relate the magnitude and phase of an input sinusoid to the correspondingly magnitude and phase of the output sinusoid.


We already did this analysis, which gave that

$$M(\omega) \equiv \frac{\text{amplitude of ss. output}}{\text{amplitude of forcing func.}} = \frac{1}{\sqrt{1+\tau^2\omega^2}} \quad \text{and} \quad \phi \equiv -\text{atan}(\tau\omega),$$



where we identify  $\tau = RC$  as the time constant.

The plots show  $M(\omega)$  and  $\phi(\omega)$ .  $\tau\omega$  is the dimensionless variable often used in these plots

 $\omega_c \equiv \frac{1}{\tau}$  is called the **cutoff frequency**. At this frequency, the magnitude ratio is  $-3$  dB. dB (decibels) are related to amplitudes through the relation



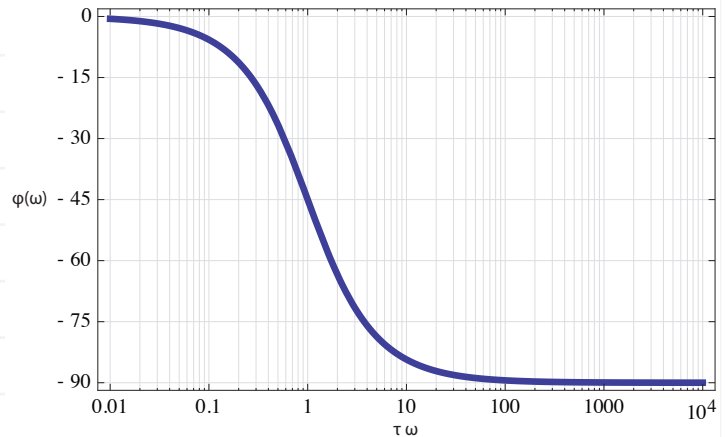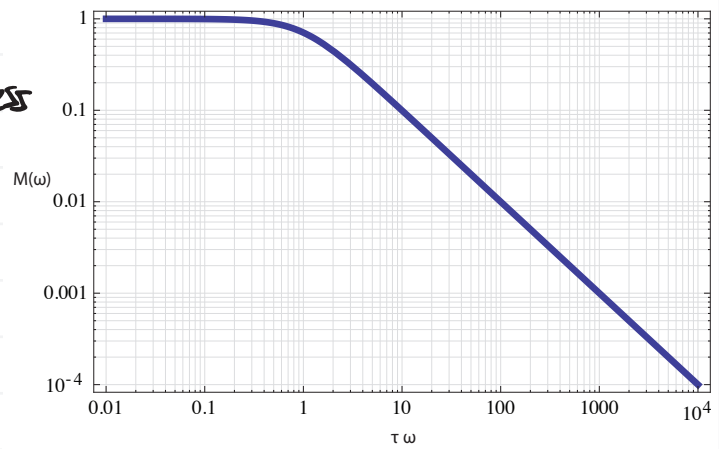The  $-3$  dB point relates to an amplitude ratio, then, of



Notice that the magnitude ratio for  $\omega < \omega_c$  is near 1, which means the output amplitude is nearly equal to the input amplitude. For  $\omega > \omega_c$ , the output amplitude is attenuated, and for  $\omega \gg \omega_c$ , it is very small. For these reasons, this circuit is called a **low-pass filter**.

The graph for  $\phi$  shows that the output **lags** the input by an amount between  $0^\circ$  and  $90^\circ$ . At the cutoff frequency  $\omega_c$ ,  $\phi(\omega_c) = -45^\circ$ .