

## Impedance

With complex representations for voltage and current, we can introduce the concept of **impedance**. Impedance  $Z$  is the complex ratio of voltage to current in a circuit element.

$$Z \equiv v/i$$

The real part is called the resistance and the imaginary part the **reactance**:

$$\text{impedance} = (\text{resistance}) + j(\text{reactance})$$

As with complex voltage and current, we can represent the impedance as a phasor.

We can use the impedance to define the **generalized Ohm's law**:

$$v = i Z$$

for each circuit element.

## Impedances of circuit elements


The impedances of the three most common circuit elements are listed below in complex forms. ( $\omega \equiv$  angular frequency)

$$\text{Resistor: } Z = R \cos 0 + j \sin 0 = R = R e^{j0} = R \angle 0$$

$$\text{Capacitor: } Z = \frac{1}{\omega C} \left( \cos \frac{-\pi}{2} + j \sin \frac{-\pi}{2} \right) = 1/(j\omega C) = \frac{1}{\omega C} e^{-j\frac{\pi}{2}} = \frac{1}{\omega C} \angle \frac{-\pi}{2}$$

$$\text{Inductor: } Z = \omega L \left( \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} \right) = j\omega L = \omega L e^{j\frac{\pi}{2}} = \omega L \angle \frac{\pi}{2}$$

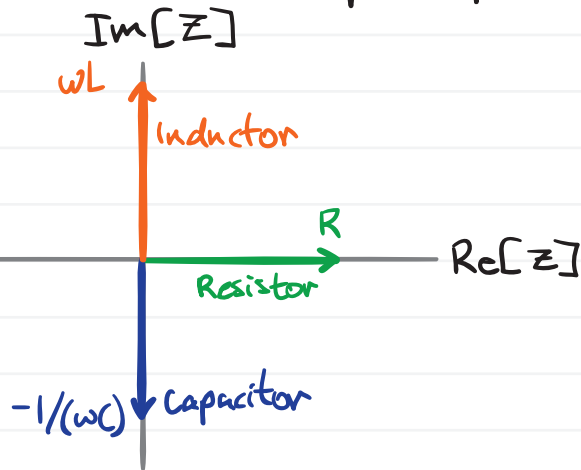Here is an illustration in the complex plane.



## Combining impedances


As with resistors, impedances may be combined to find an effective impedance. We often want to know the effective impedance of a circuit or portion thereof.

Series impedances can be combined in the following manner:



$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n = \sum_{k=1}^n Z_k$$

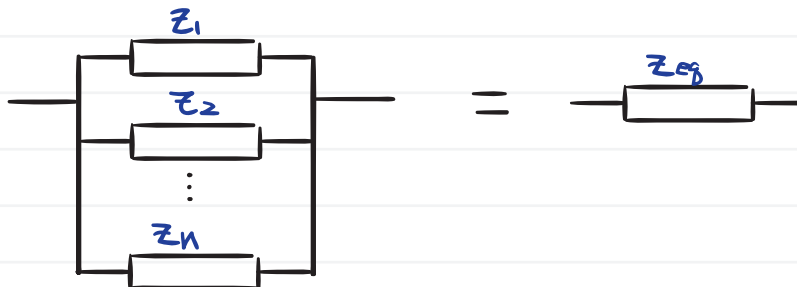Parallel impedances can be combined in the following manner:



$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}} = 1 / \sum_{k=1}^n 1/Z_k$$