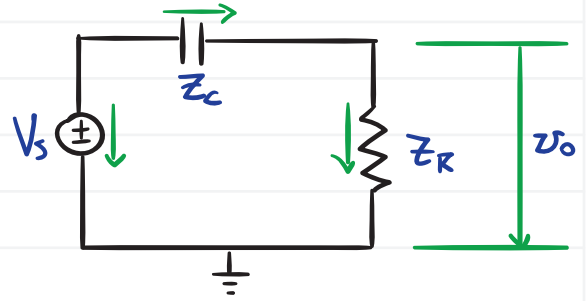


# Complex circuit analysis of a differentiator (example)

Given the differentiator circuit shown, with  $V_s(t) = A \cos(\omega t)$ , what is  $v_o$  in the steady-state?



1. Sign convention.

2. Since there is a sinusoidal input and we are concerned about steady-state behavior, we can use impedance analysis. The elemental equation of each passive element is given by the generalized Ohm's law:

— Resistor:  $v_R = i_R Z_R = i_R R$

— Capacitor:  $v_C = i_C Z_C = i_C \frac{1}{\omega C} e^{-j\frac{\pi}{2}}$

3. KCL:  $i_C = i_R = i$

4. KVL:  $V_s = v_C + v_R$

5. Complex algebra. We want  $v_o = v_R$ . Therefore,

$$v_o = V_s - v_C = A - i \frac{1}{\omega C} e^{-j\frac{\pi}{2}} = A - \frac{v_o}{R} \frac{1}{\omega C} e^{-j\frac{\pi}{2}}$$

$$\begin{aligned} \Rightarrow v_o &= A / \left( 1 + \frac{1}{RC\omega} e^{-j\frac{\pi}{2}} \right) = A / \left( 1 + \frac{1}{RC\omega} (\cos \frac{\pi}{2} + j \sin \frac{\pi}{2}) \right) \\ &= A / \left( 1 - j \frac{1}{RC\omega} \right) = A / \left( \sqrt{1^2 + \left( \frac{1}{RC\omega} \right)^2} e^{j\phi} \right) \quad \left| \phi \equiv \arctan \left( \frac{-\frac{1}{RC\omega}}{1} \right) \right. \\ &= \frac{ARC\omega}{\sqrt{(RC\omega)^2 + 1}} e^{j\phi} = \frac{A\omega}{\sqrt{\omega^2 + 1/(RC)^2}} \cos(\omega t - \phi) \end{aligned}$$