

Complex circuit analysis of a differentiator (example)

Given the differentiator circuit shown, with $v_s(t) = A \cos(\omega t)$, what is v_o in the steady-state?

