

## DC motor and battery

Two common DC circuit elements are batteries and DC motors. We will model each.

### DC motors

DC motors exert a torque  $T = k_t i$  (where  $k_t$  is the torque motor constant and  $i$  is the motor current) on a rotational mechanical load.

A motor's **armature** is typically a wire coil through which current flows. A magnetic field is applied such that the coil rotates due to its magnetic field interaction (called the Lorentz force).

The resistor  $R$  and inductor  $L$  account for the armature's resistance + inductance.


The mysterious voltage source  $V_{emf}$  is called the **counter-emf** or **back-emf**. As the motor speeds up, Faraday's Law predicts

a voltage will be generated in opposition to the original (no velocity) voltage. This behavior is that which makes a motor behave as a generator.

The motor constants  $K_t + K_v$  are usually provided by the manufacturer of the motor.

Assuming steady-state operation (i.e. DC current applied), we can ignore the inductance  $L$ . The current  $i$  is of primary importance to us so we compute it:

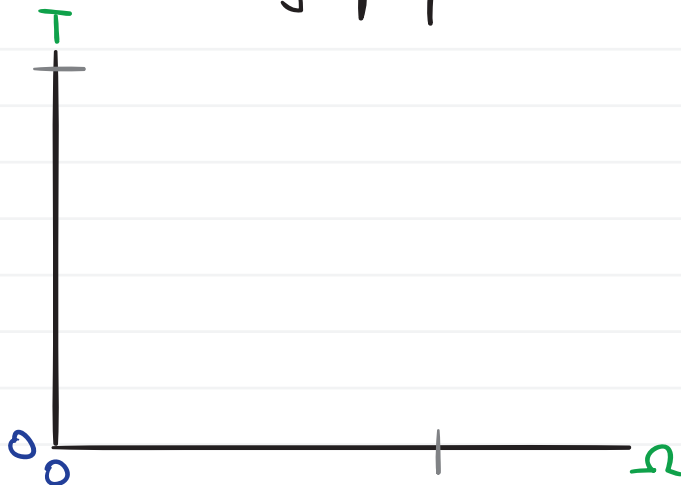This relationship predicts the familiar result that motor torque and speed are inversely proportional



## Batteries

A battery can be modeled as an ideal voltage source in series with a resistor.

The battery's internal resistance yields the output voltages:

no load:

load: