

## 13.1 imp.ip Input impedance and admittance


- 1 We now introduce a generalization of the familiar impedance and admittance of electrical circuit analysis, in which system behavior can be expressed algebraically instead of differentially. We begin with generalized input impedance.
- 2 Consider a system with a source, as shown in Fig. ip.1. The source can be either an across- or a through-variable source. The ideal source specifies either  $\mathcal{V}_{in}$  or  $\mathcal{F}_{in}$ , and the other variable depends on the system.
- 3 Let a source variables have Laplace transforms  $\mathcal{V}_{in}(s)$  and  $\mathcal{F}_{in}(s)$ . We define the system's **input impedance**  $Z$  and **input admittance**  $Y$  to be the Laplace-domain ratios

$$Z(s) = \frac{\mathcal{V}_{in}(s)}{\mathcal{F}_{in}(s)} \quad \text{and} \quad Y(s) = \frac{\mathcal{F}_{in}(s)}{\mathcal{V}_{in}(s)}. \quad (1)$$

Clearly,



Both  $Z$  and  $Y$  can be considered **transfer functions**: for a through-variable source  $\mathcal{F}_{in}$ , the impedance  $Z$  is the transfer function to across-variable  $\mathcal{V}_{in}$ ; for an across-variable source  $\mathcal{V}_{in}$ , the admittance  $Y$  is the transfer function to through-variable  $\mathcal{F}_{in}$ . Often, however, we use the more common impedance  $Z$  to characterize systems with either type of source.

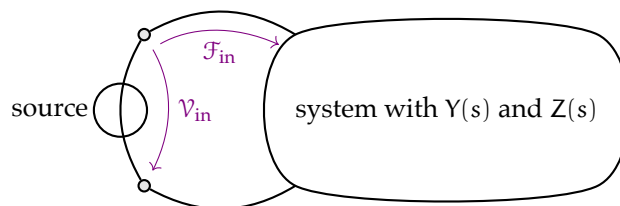

**Figure ip.1:**

4 Note that  $Z$  and  $Y$  are **system properties**, not properties of the source. An impedance or admittance can characterize a system of interconnected elements, or a system of a single element, as the next section explores.

### Impedance of ideal passive elements

5 The impedance and admittance of a single, ideal, one-port element is defined from the Laplace transform of its elemental equation.

**Generalized capacitors** A **generalized capacitor** has elemental equation

$$\frac{d\mathcal{V}_C(t)}{dt} = \frac{1}{C}\mathcal{F}_C(t), \quad (2)$$

the Laplace transform of which is

$$s\mathcal{V}_C(s) = \frac{1}{C}\mathcal{F}_C(s), \quad (3)$$

which can be solved for impedance  $Z_C = \mathcal{V}_C/\mathcal{F}_C$  and admittance  $Y_C = \mathcal{F}_C/\mathcal{V}_C$ :




**Generalized inductors** A **generalized inductor** has elemental equation

$$\frac{d\mathcal{F}_L(t)}{dt} = \frac{1}{L}\mathcal{V}_L(t), \quad (4)$$

the Laplace transform of which is

$$s\mathcal{F}_L(s) = \frac{1}{L}\mathcal{V}_L(s), \quad (5)$$

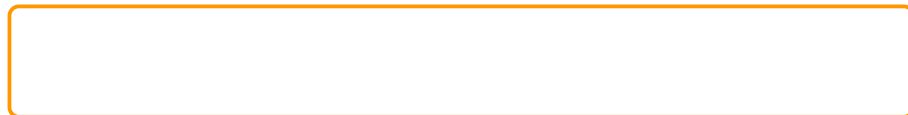which can be solved for impedance  $Z_L = \mathcal{V}_L/\mathcal{F}_L$  and admittance  $Y_L = \mathcal{F}_L/\mathcal{V}_L$ :



**Generalized resistors** A **generalized resistor** has elemental equation

$$\mathcal{V}_R(t) = \mathcal{F}_R(t)R, \tag{6}$$

the Laplace transform of which is

$$\mathcal{V}_R(s) = \mathcal{F}_R(s)R, \tag{7}$$


which can be solved for impedance  $Z_R = \mathcal{V}_R/\mathcal{F}_R$  and admittance  $Y_R = \mathcal{F}_R/\mathcal{V}_R$ :




6 For a summary of the impedance of one-port elements, see [Table els.1](#).

**Impedance of interconnected elements**

7 As with electrical circuits, impedances of linear graphs of interconnected elements can be combined in two primary ways: in parallel or in series.

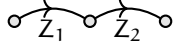8 Elements sharing the same through-variable are said to be in **series** connection. N elements connected in series  ... have equivalent impedance Z and admittance Y:


$$Z(s) = \sum_{i=1}^N Z_i(s) \quad \text{and} \quad Y(s) = 1 / \sum_{i=1}^N 1/Y_i(s) \tag{8}$$

9 Conversely, elements sharing the same across-variable are said to be in **parallel** connection. N elements connected in parallel  ... have equivalent impedance Z and admittance Y:

$$Z(s) = 1 / \sum_{i=1}^N 1/Z_i(s) \quad \text{and} \quad Y(s) = \sum_{i=1}^N Y_i(s). \tag{9}$$

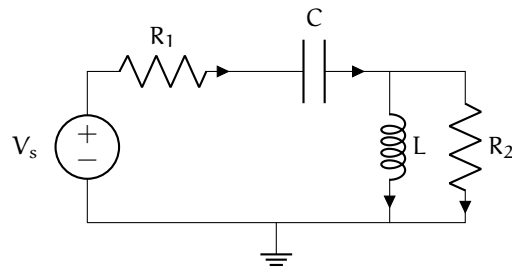**Example 13.1 imp.ip-1**

For the circuit shown, find the input impedance.



re:  
input  
impedance  
of a  
simple  
circuit