

13.5 imp.equiv Norton and Thévenin theorems

1 The following remarkable theorem has been proven.⁵

Theorem 13 imp.1: generalized Thévenin's theorem

Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single *across-variable source* \mathcal{V}_e in series with an impedance Z_e .

2 The equivalent linear network has two quantities to determine: \mathcal{V}_e and Z_e .

Determining Z_e

3 The **equivalent impedance** Z_e of a network is the impedance between the output nodes with all inputs set to zero. Setting an across-variable source to zero means the across-variable on both its terminals are equal, which is equivalent to treating them as the same node. Setting a through-variable source to zero means the through-variable through it is zero, which is equivalent to treating its nodes as disconnected.

Determining \mathcal{V}_e

4 The **equivalent across-variable source** \mathcal{V}_e is the across-variable at the output nodes of the network when they are left open (disconnected from a load). Determining this value typically requires some analysis with the elemental, continuity, and compatibility equations (preferably via impedance methods).

Norton's theorem

5 Similarly, the following remarkable theorem has been proven.

⁵This lecture is intentionally strongly paralleled in our *Electronics* lecture on Norton's and Thévenin's theorems.

Theorem 13 imp.2: generalized Norton's theorem

Given a linear network of across-variable sources, through-variable sources, and impedances, the behavior at the network's output nodes can be reproduced exactly by a single *through-variable source* \mathcal{F}_e in parallel with an impedance Z_e .

6 The equivalent network has two quantities to determine: \mathcal{F}_e and Z_e . The equivalent impedance Z_e is identical to that of Thévenin's theorem, which leaves the equivalent through-variable source \mathcal{F}_e to be determined.

Determining \mathcal{F}_e

7 The **equivalent through-variable source** \mathcal{F}_e is the through-variable through the output terminals of the network when they are shorted (collapsed to a single node). Determining this value typically requires some analysis with elemental, continuity, and compatibility equations (preferably via impedance methods).


Converting between Thévenin and Norton equivalents

8 There is an equivalence between the two equivalent network models that allows one to convert from one to another with ease. The equivalent impedance Z_e is identical in each and provides the following equation for converting between the two representations:

Equation 1 converting between Thévenin and Norton equivalents

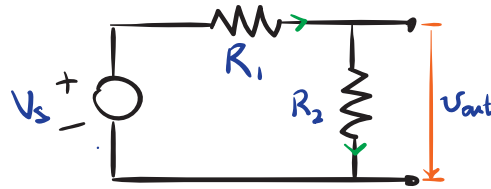Example 13.5 imp.equiv-1

For the circuit shown, find a Thévenin and a Norton equivalent.



re:
Thévenin
and
Norton
equivalents