

02.3 can.exa A sinusoidal input example


Notice that we have yet to talk about **alternating current (ac) circuit analysis** or **direct current (dc) circuit analysis**. In fact, these ambiguous terms can mean a few different things. Approximately, an ac circuit analysis is one for which the input is sinusoidal and a dc circuit analysis is one for which the input is a constant. This ignores **transient response** (early response when the initial-condition response dominates) versus **steady-state response** (later response when the initial-condition response has decayed) considerations. We'll consider this more in [Lec. 02.4 can.trss](#).

We have remained general enough to be able to handle sinusoidal and constant sources in both transient and steady-state response.

[Example 02.2 can.mthd-1](#) features a circuit with a constant voltage source and a capacitor. Now we consider circuit with a sinusoidal current source and an inductor because why change only one thing when you could change more?

Example 02.3 can.exa-1

Given the RL circuit shown, current input $I_s(t) = A \sin \omega t$, and initial condition $i_L(t)|_{t=0} = i_0$, what are $i_L(t)$ and $v_L(t)$ for $t \geq 0$?

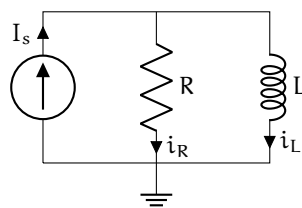

re: RL circuit analysis with a sinusoidal source



