

### Lecture 05.03 Boolean algebra on digital signals

We will require an understanding of Boolean algebra on digital signals to implement a switch debouncing circuit in [Lecture 05.04](#). It is a digital circuit that operates with logic gates, which are here introduced.


propositional  
calculus  
Boolean algebra  
truth table

A digital signal's Boolean variable values 1 and 0 are isomorphic to *propositional calculus's* truth values  $\top$  (true) and  $\perp$  (false). Similarly, *Boolean algebra* (i.e. Boolean logic) operations are isomorphic to propositional calculus operations, such as *not* ( $\neg$ ), *and* ( $\wedge$ ), and *or* ( $\vee$ ). [Table 05.1](#) is a *truth table* for a number of Boolean algebra operators.

logic gates

Digital electronics instantiate these operators as *logic gates*, sometimes as subcircuits of CPUs and sometimes as discrete integrated circuits for incorporation on a prototyping board (as in [Lab Exercise 05](#)) and eventually on a PCB. The simplest gate is the *not gate*, which has the following circuit symbol.


not gate

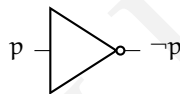

This gate accepts digital signal represented by Boolean variable  $p$  and returns  $\neg p$ . So,  $p = 1 \Rightarrow \neg p = 0$  and  $p = 0 \Rightarrow \neg p = 1$ .

or gate








Most gates have two inputs. For instance, the *or gate*, what has circuit symbol

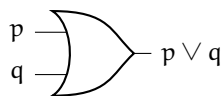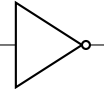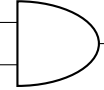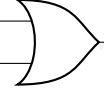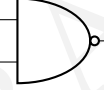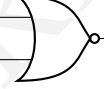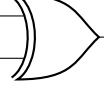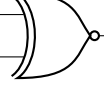

**Table 05.1:** a truth table for logic operations. The first two columns are operation *inputs*, the rest, *outputs*.

		not	and	or	nand	nor	xor	xnor
p	q	$\neg p$	$p \wedge q$	$p \vee q$	$p \uparrow q$	$p \downarrow q$	$p \nabla q$	$p \Leftrightarrow q$
0	0	1	0	0	1	1	0	1
0	1	1	0	1	1	0	1	0
1	0	0	0	1	1	0	1	0
1	1	0	1	1	0	0	0	1

**Table 05.2:** logic operations and equivalent C expressions and gate symbols.

name	logic	C	gate
not	$\neg p$	!p	
and	$p \wedge q$	p&&q	
or	$p \vee q$	p  q	
nand	$p \uparrow q$	!(p&&q)	
nor	$p \downarrow q$	!(p  q)	
xor	$p \underline{\vee} q$	p!=q	
xnor	$p \Leftrightarrow q$	p==q	

accepts digital signals with Boolean variables (say)  $p$  and  $q$  and returns  $p \vee q$ . Table 05.2 summarizes logic gates and their associated Boolean algebra operators.